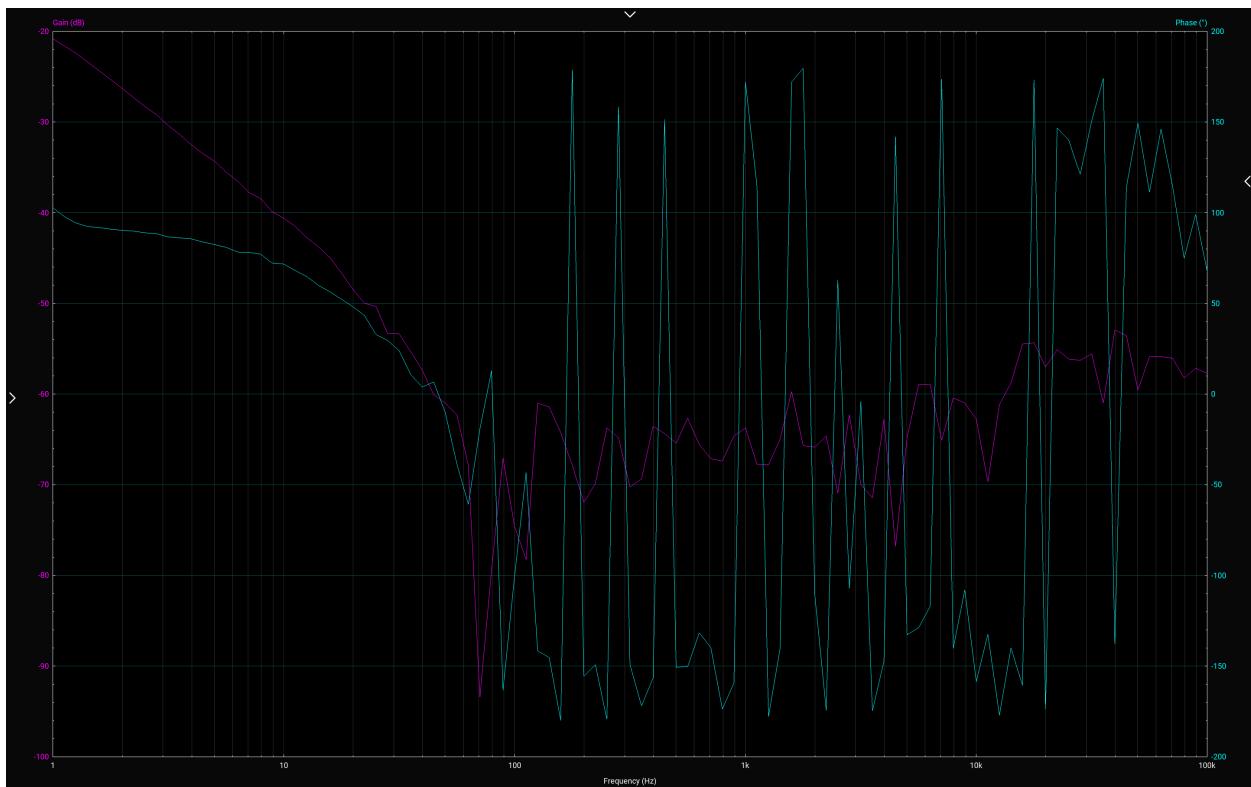



Lab 5

A Bode plot (Amplitude only)

Caption: This Bode Plot represents a low pass filter at a frequency beginning at 1 Hz. X-axis is labelled as Frequency in terms of Hz. Y-axis is in terms of dB where I used the amplitude formula to confirm the values (attached picture with my calculations and amplitude photo).



Picture of breadboard

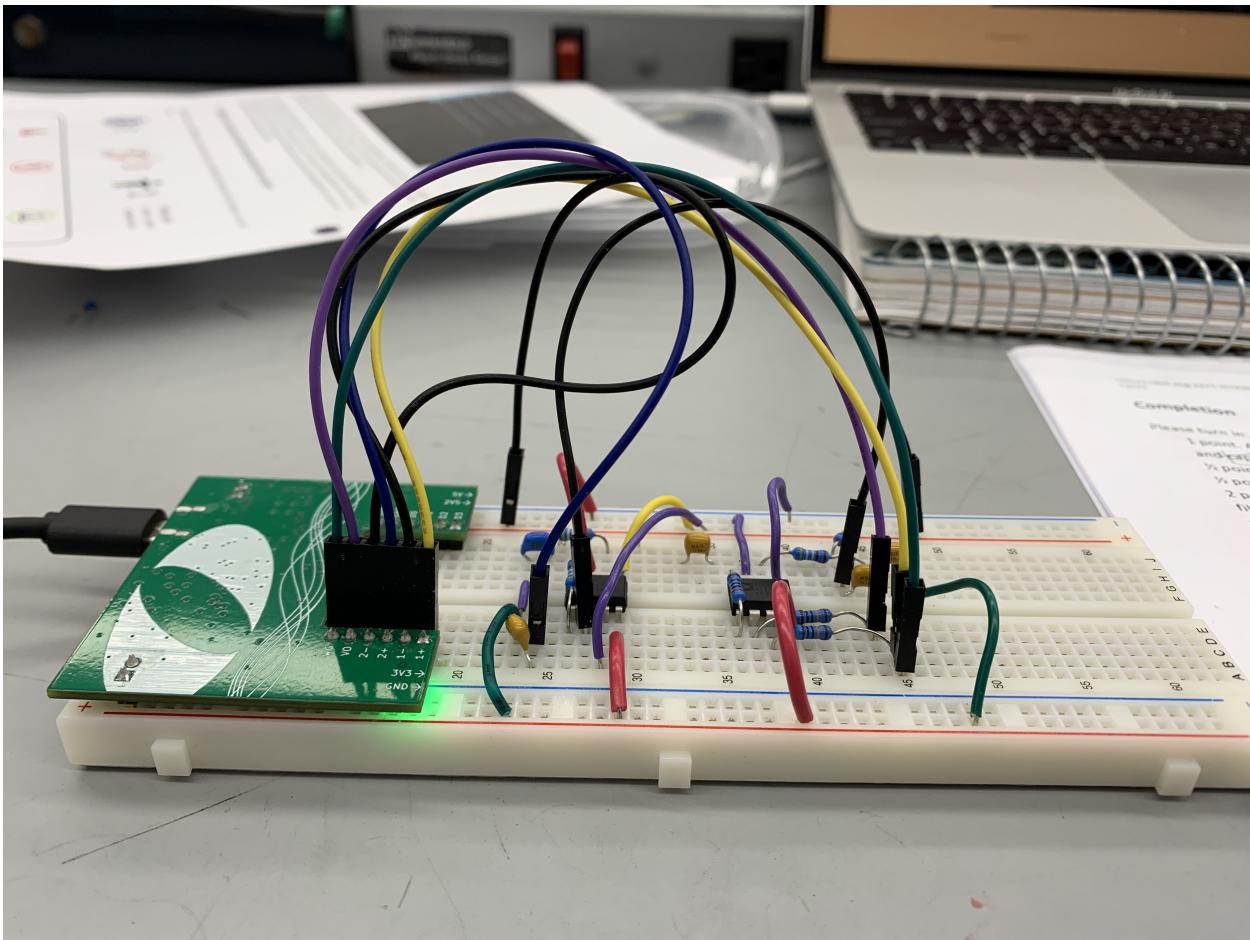

Describe how the circuit functions

Included in photo: characteristic frequency calculation, amplifier gains (definitions and calculations), circuit filters (schematics and total filters).

- Why do we multiply amplifier gains?

Multiply the amplifying gains because one output (output from circuit 1) is the input to the second output (circuit 2). \rightarrow Cuit 1:

Amplifier gains

$$1 + \frac{100k\Omega}{2k\Omega}$$

$$1 + \frac{100k\Omega}{4.9k\Omega}$$

- What does the amplifier gain mean?

Amplifying gain is the # for how much the output voltage is amplified. The only amplifying voltage and current. For resistors, we'd increase our resistor value.

Characteristic frequency

Meaning: This is the frequency when the filter begins to attenuate or pass signals.

$$f_c = \frac{1}{2\pi(400)(0.00001)} \quad \text{second stage filter}$$

$\rightarrow 31.9\text{Hz}$. The configuration of this makes it a low pass filter so values/frequencies below 31.9Hz will be passed.

$$f_c = \frac{1}{2\pi(4900)(0.00001)} = 32.5\text{Hz} \quad \text{second stage filter}$$

